

Please check that this question paper contains 9 questions and 2 printed pages within first ten minutes.

[Total No. of Questions: 09]

[Total No. of Pages: 2...]

Uni. Roll No. ....

Program: B.Tech. (Batch 2018 onward)

Semester:.....3rd.....

MORNING

Name of Subject: Digital Circuits and Logic Design

09 MAY 2023

Subject Code: ...ESIT-101.....

Paper ID: ...16042....

Scientific calculator is Allowed

**Time Allowed: 03 Hours**

**Max. Marks: 60**

**NOTE:**

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

**Part – A**

**[Marks: 02 each]**

**Q1.**

- Q1. a) What are ASCII codes.
- b) What is the difference between Multiplexer and Demultiplexer.
- c) Differentiate between Flip flop and Register.
- d) Give the use of VHDL.
- e) State and prove De Morgan's theorem.
- f) Why NAND and NOR are called universal gates?

**Part – B**

**[Marks: 04 each]**

Q2) Why Gray codes are used in K-Maps. Explain in detail

Q3) Convert the following:

- a)  $(331)_8 = ( )_{16} = ( )_{10}$
- b)  $(11001010)_2 = ( )_{\text{Gray code}}$
- c)  $(111)_2 = ( )_{\text{BCD}}$
- d)  $(1101)_2 + (1110)_2 = ( )_8$

Q4) Simplify following expressions using Boolean algebra

a)  $F(P,Q,R)=P'Q+QR'+QR+PQ'R'$

b)  $F(X,Y,Z)=X'Y'Z'+X'YZ'+X'YZ+XYZ'$

MORNING  
09 MAY 2023

Q5) What is SOP and POS in digital circuits? Explain in detail.

Q6) Using Universal gates, create following gates

a) XOR      b) AND

Q7) Design 2 bit Encoder and Decoder circuit

**Part – C**

[Marks: 12 each]

Q8) Design 3 bit Synchronous Up Counter.

OR

Simplify the given K-Map

ab cd	00	01	11	10
00	1	X	X	1
01	X			1
11				
10	1			X

Q9) What are various techniques to convert Analog to Digital signals? Explain any one in detail.

OR

Demonstrate the working of Master Slave flip-flop in detail.

\*\*\*\*\*